

COMPLEMENTARY PULLUPS AND PULLDOWNS

This is what the "C" in CMOS stands for!

We design components with complementary pullup and pulldown logic (i.e., the pulldown should be "on" when the pullup is "off" and vice versa).

pullup	pulldown	F(I,,I)
on	off	driven "1"
off	on	driven "0" Convention: In general
on	on	driven "X" - driven ast
off	off	no connection When they are used, the resulting device is not STRICTLY following our

SIVITC DISCTATINE (eq. Pass gates and storage devices).

Such devices are only QUASI-DIGITALI





A TWO-INPUT LOGIC GATE



HERE'S ANOTHER ...





What function does this gate compute?

Α	B	С
0	0	
0	1	
1	0	
1	1	

GENERAL CMOS GATE RECIPE

Step 1. Figure out pulldown network that does what you want (i.e the set of conditions where the output is 'O') e.g., $F = \overline{A \&\& (B \parallel C)}$

Step 2. Walk the hierarchy replacing nfets with pfets, series subnets with parallel subnets, and parallel subnets with series subnets

Step 3. Combine pfet pullup network from Step 2 with nfet pulldown network from Step 1 to form fully-complementary CMOS gate.









ONE LAST EXERCISE

Let's construct a gate to compute:

 $F = \overline{A \parallel (B \& \& C)} = NOT(OR(A, AND(B, C)))$





ANDROID

NOTDROID

DRDROID

NANDROID

7

Now that we can see what goes on inside of a single gate, we'll next use several them to compose larger systems that compute other logic functions.

NEXT TIME



MIDTERM PRACTICE



Which of the following ARM instructions might be encoded as: 0x03A01008?

O Idreq r1,[r3,#10]

O Idreq r1,x

O bxeq r1

- O bleq main
- moveq r1,#x

MIDTERM PRACTICE



4 points

Shown below is a complete set of double-six domino tiles. Suppose someone tells you that a tile they are holding has a 5 spot. How many bits of information are conveyed?



log2(28/5)

log2(28/7)

log2(28/8)

log2(28/9)

None of the above

MIDTERM PRACTICE



If an ASCII character array containing "EDIT" appears in a 4 points word of memory as 0x54494445, what can you infer?

- The computer is using a convention where all strings are aligned to word boundaries
- O The letter "E" is encoded in ascii as 01010100
- O The machine is byte addressable
- O The machine uses little-endian addressing

All of the above

ENUMERATING AND COMPOSING GATES



- Combinational logic as/is truth tables
- Composing gates
- What gates do we have?
- What gates do we need?
- Making gates from others
- A systematic approach for implementing combinational logic

Midterm #1 on Friday



NOW CAN WE DESIGN LARGER SYSTEMS

We need to start somewhere -

usually with a functional specification



Argh... I'm tired of word games

Truth Table

С	В	A	У
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

If you are like most pragmatists you'd rather be given a table or formula than solve a puzzle to understand a function. The fact is, every combinational function can be expressed as a table.

"Truth tables" are a concise description of the combinational system's function, where an output is specified for *every* input combination.

TRUTH TABLES TO GATES?



We want to build a computer!



So far we know how to build a few CMOS gates using MOSFET transistors

(NAND, NOR, INVERTER)

But we are missing AND, OR, and XOR

What gates can we build using CMOS?

WHAT GATES CAN WE BUILD?



Recall, we need to design our gates using a pull-up network of P-FETs and a pull-down network of N-FETs.

What gates can we	AN	JD	Ο	R	NA	ND	NC	DR
- build?	AB	У	AB	У	AB	У	AB	У
- define?	00	0	00	0	00	1	00	1
l et's stort by	01	0	01	1	01	1	01	0
concidering only	10	0	10	1	10	1	10	0
2 input actor	11	1	11	1	11	0	11	0
2-input gates.		•		•	_			•

How many possible 2-input gates are there? KEY IDEA: As many as there are 2-input truth tables. 2-inputs $\rightarrow 2^2 = 4$ rows, each with an output 4-outputs $\rightarrow 2^4 = 16$ possible functions

Comp 411 - Fall 2017

ALL THE GATES



There are only 16 possible 2-input gates... Let's examine all of them. Some we already know, others are just silly.



How many of these gates can be implemented using a single CMOS gate?

> N-FETs can only pull the ouput to "0", and only if one or more of their inputs is a "1".

P-FETs can only pull the ouput to "I", and only if one or more of their inputs is a "O".

Do we really need all of these gates?

Nope! Once we realize that we can describe all of them using just AND, OR, and NOT

COMPOSING GATES TO BUILD OTHERS



Let's start with a couple of basics, AND and OR. Each can be constructed using a pair of CMOS gates, AND is just NAND with an inverter, and OR is just NOR with an inverted output.



Comp 411 - Fall 2017



COMPOSING ARBITRARY GATES



How many different gates do we really need?

We can always do it with 3 different types of gates (AND, OR, INVERT), and sometimes with 2, but, can we use fewer? The TRICK is to OR the ANDs of all input combinations that generate an output of "I". You don't need the OR gate if only one input combination results in a "I".

You need Inverters to handle input combinations involving "0"s, ANDs, and ORs.

ONE WILL DO!

NANDs and NORs are UNIVERSAL!

A UNIVERSAL gate is one that can be used to implement *ANY* COMBINATIONAL FUNCTION. There are many UNIVERSAL gates, but not all gates are UNIVERSAL



Q: What is a COMBINATIONAL FUNCTION? A: Any function that can be written as a truth table.



Ah!, but what if we want more than 2-inputs?

STUPID GATE TRICKS







output = 1 iff number of "1"s input is ODD ("PARITY")

t_{nd} = N nS -- WORST CASE.

Can we compute an N-input XOR faster?



I THINK THAT I SHALL NEVER SEE

A GATE LOVELY AS A ...

EVERY N-Input Combinational function be implemented using only 2-input gates? But, it's handy to have gates with more than 2-inputs when log₂N N-input TREE has O(log N) levels... needed. Signal propagation takes O(log N_) gate delays.

A SYSTEMATIC DESIGN APPROACH



Truth Table

С	В	A	У		
0	0	0	0		
0	0	1	1		
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		
-it's systematic!					

-it's easy!

10/09/2017

-we get to go home!

1) Write the functional spec as a truth table

- 2) Write down a Boolean expression for every "in the output
 - Y = (!C && !B && A) || (!C && B && A) || (C && B && !A) || (C && B && A)
- 3) Wire up the ideal gates, replace them with equivalent realizable gates, call it a day, and go home!

This approach will always give us logic expressions in a particular form: SUM-OF-PRODUCTS



STRAIGHTFORWARD SYNTHESIS

We can implement

SUM-OF-PRODUCTS

with just 3 levels of logic.

INVERTERS/AND/OR





OTHER USEFUL CMOS GATES

AOI (AND-OR-INVERT)



OAI (OR-AND-INVERT)

Β

B





AOI and OAI structures can be realized as a single CMOS gate. However, their function is equivalent to 3 levels of logic.

An OAI's DeMorgan equivalent is usually easier to think about.





AN INTERESTING 3-INPUT GATE



Based on C, select the A or B input to be copied to Y.





MUX COMPOSITIONS AND SHORTCUTS





A 4-bit wide 2-input Mux





MUX FUNCTION SYNTHESIS



Consider implementation of some arbitrary Combinational function, F(A,B,C)... using a MULTIPLEXER as the only circuit element:



Comp 411 - Fall 2017

MUX LOGIC TRICKS



We can apply certain optimizations to MUX Function synthesis



NEXT TIME

Binary Circuits that: ADD SUBTRACT SHIFT



