
 




LATCHES: DIGITAL STORAGE ELEMENTS

 

Positive latch



Negative latch

  


Latches are a digital "memory", they "remember" one-bit while their "gate", G , is closed. When open, their output follows the input D . The last value of D is remembered when the gate is closed.

ONE GATE IS NOT ENOUGH



 It is difficult to control precisely how long a gate should be opened to allow exactly one data value to get through.




TWO GATES PROVIDE PRECISE CONTROL



The Solution:

 
With two gates, where only one is open at any time, we can allow only the desired data through





EDGE-TRIGGERED FLIP FLOP

LOGICAL "ESCAPEMENT"

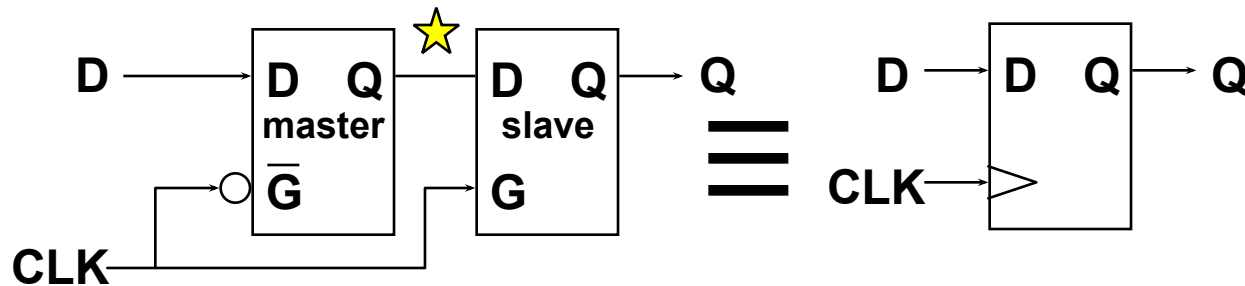


Observations:

- only one latch's gate is open at any time
- master closed when slave is open (CLK is high)
- slave closed when master is open (CLK is low)
- no combinational path through flip flop
- Q only changes shortly after 0→1 transition of CLK, so a "flip flop" appears to be "triggered" by rising edge of CLK


Transitions mark
instants, not
intervals



FLIP-FLOP TIMING

 

 The output of a flip-flop only changes after the rising edge of its clock




master closed
slave open

slave closed
master open





TWO ISSUES

 

- Must allow time for the input's value to propagate to the Master's output while CLK is LOW.
 - This is called "SET-UP" time (How long a D input must valid before the clock rises)
- Must keep the input stable, just after CLK transitions to HIGH. This is insurance in case the SLAVE's gate opens just before the MASTER's gate closes.
 - This is called "HOLD-TIME" (How long a D input must "remain" valid after the clock rises)
 - Can be zero (or even negative!)
- Assuring "set-up" and "hold" times is what limits a computer's performance



FLIP-FLOP TIMING SPECS

  

t_{PD} : maximum propagation delay, CLK \rightarrow Q

t_{SETUP} : setup time

guarantee that D has propagated through feedback path before master closes

t_{HOLD} : hold time

guarantee master is closed and data is stable before allowing D to change

SUMMARY





- Regular Arrays can be used to implement arbitrary logic functions
- ROMs decode every input combination (fixed-AND array) and compute the output for it (customized-OR array)
- Memories
 - ROMs are HARDWIRED memories
 - RAMs include storage elements at each WORD-line and BIT-line intersection
 - dynamic memory: compact, only reliable short-term
 - static memory: controlled use of positive feedback
- Level-sensitive D-latches for static storage
- Dynamic discipline (setup and hold times)


SYNCHRONOUS LOGIC



  - 1) Sequential Logic
- 2) Synchronous Design
- 3) Synchronous Timing Analysis
- 4) Single Clock Design
- 5) Finite State Machines
- 6) Mealy and Moore
- 7) State Transition Diagrams



ROAD TRAVELED SO FAR...

 

Combinational contract:

- Voltage-based "bits"
- 1-bit per wire
- Generate quality outputs, tolerate inferior inputs
- Combinational contract
- Complete in/out/timing spec

Acyclic connections

Composable blocks

Design:

- truth tables
- sum-of-products
- muxes
- ROMs

Storage & state

Dynamic discipline

Finite-state machines

Throughput & latency


Pipelining

Our motto: Sweat the details once, and then put a box around it!

SOMETHING WE CAN'T BUILD



 
What if you were given the following system design specification?



What makes this System so different from those we've discussed before?

1. "State" - i.e. the circuit has memory
2. The output was changed by an input "event" (pushing a button) rather than an input "value"


"SEQUENTIAL" = STATEFUL

 


Plan: Build a Sequential Circuit with stored digital STATE -

- MEMORY stores CURRENT state
- Combinational Logic computes
 - the NEXT state (Based on inputs & current state)
 - the OUTPUTs (Based on inputs and/or current state)
 - State changes on LOAD control input

 Didn't we develop
some memory
devices last time?




"SYNCHRONOUS" SINGLE-CLOCK LOGIC

 

 Questions for register-based designs:

- How much time for useful work (i.e. for combinational logic delay)?

- Does it help to guarantee a minimum t_{CD} ? How 'bout designing registers so that $t_{CD,reg} \geq t_{HOLD,reg}$?




- What happens if CLK signal doesn't arrive at the two registers at exactly the same time (a phenomenon known as "clock skew")?

$$t_1 = t_{CD,reg1} + t_{CD,L} \geq t_{HOLD,reg2}$$

$$t_2 = t_{PD,reg1} + t_{PD,L} \leq t_{CLK} - t_{SETUP,reg2}$$

$$\text{Minimum Clock Period : } t_{CLK} \geq t_{PD,reg1} + t_{PD,L} + t_{SETUP,reg2}$$

EXAMPLE: SYNCHRONOUS TIMING

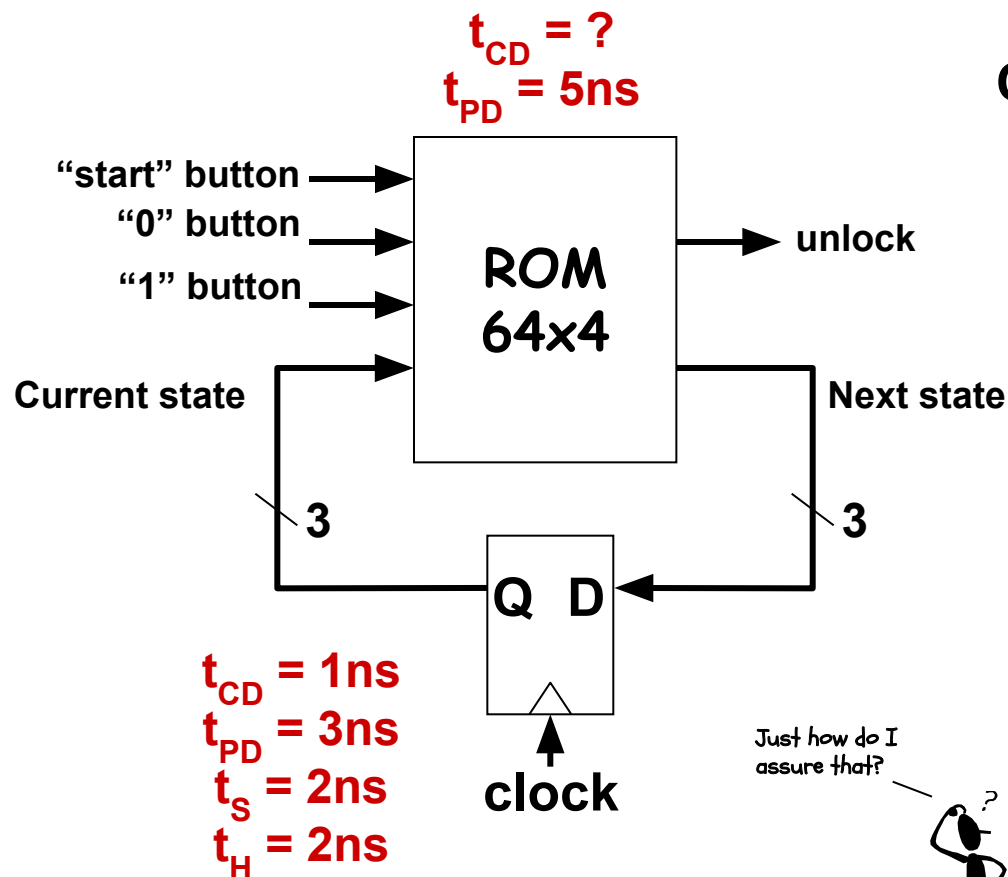

Questions:

1. t_{CD} for the ROM?

$$t_{CD,REG} + t_{CD,ROM} > t_{H,REG}$$

$$1ns + t_{CD,ROM} > 2ns$$

$$t_{CD,ROM} > 1ns$$

2. Min. clock period?

$$t_{CLK} > t_{PD,REG} + t_{PD,ROM} + t_{S,REG}$$

$$t_{CLK} > 3ns + 5ns + 2ns$$

$$t_{CLK} > 10ns$$

3. Constraints on inputs?

"start", "0", and "1" must be valid

$t_{PD,ROM} + t_{S,REG} = 5 + 2 = 7ns$
before the clock and held

$t_{H,REG} - t_{CD,ROM} = 2 - 1 = 1ns$
after it.

Just how do I
assure that?




SYNCHRONOUS SINGLE-CLOCK DESIGN



Sequential \neq Synchronous

 However, Synchronous = A recipe for robust sequential circuits:



- No combinational cycles
(other than those already inside the registers)
- Only cares about values of combinational circuits just before rising edge of clock
- Clock period greater than every combinational delay
- Changes state after all logic transitions have stopped!

DESIGNING SEQUENTIAL LOGIC



Sequential logic is used when the solution to some design problem involves a *sequence* of steps:

How to open digital combination lock w/ 3 buttons ("start", "0" and "1"):

Step 1: press "start" button

Step 2: press "0" button


Step 3: press "1" button

Step 4: press "1" button

Step 5: press "0" button



 Information remembered between steps is called **state**. Might be just what step we're on, or might include results from earlier steps we'll need to complete a later step.



IMPLEMENTING A "STATE MACHINE"



This flavor of
'truth-table' is
called a
'state-transition
table'


This is starting
to look like a
PROGRAM




Current State "start" "1" "0"					Next State unlock		
---		1	---	---	start	0	000
start	000	0	0	1	digit1	0	001
start	000	0	1	0	error	0	101
start	000	0	0	0	start	0	000
digit1	001	0	1	0	digit2	0	010
digit1	001	0	0	1	error	0	101
digit1	001	0	0	0	digit1	0	001
digit2	010	0	1	0	digit3	0	011
...							
digit3	011	0	0	1	unlock	0	100
...							
unlock	100	0	1	0	error	1	101
unlock	100	0	0	1	error	1	101
unlock	100	0	0	0	unlock	1	100
error	101	0	---	---	error	0	101

6 different states → encode using 3 bits

NOW, WE DO IT WITH HARDWARE!

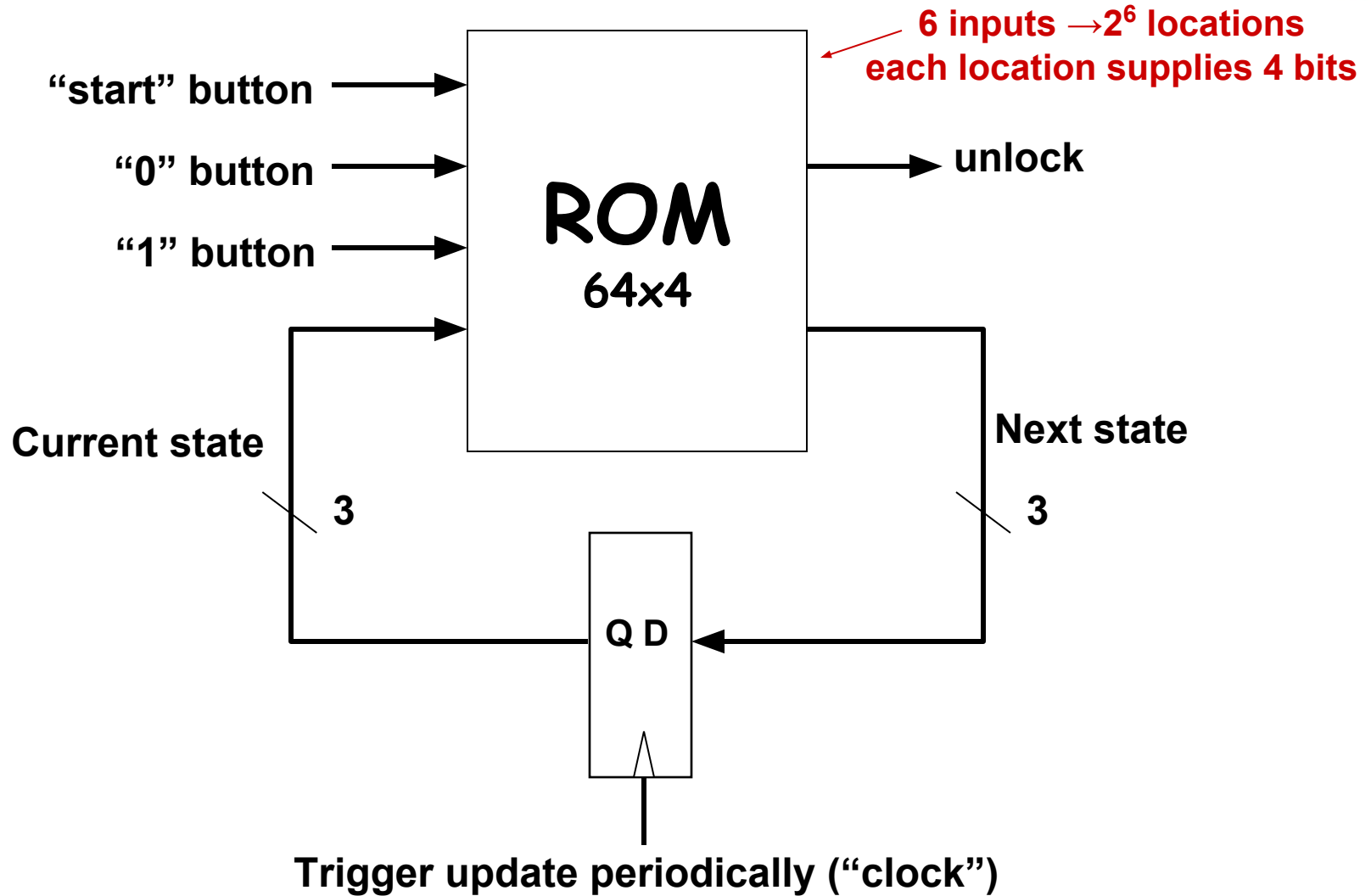


A FINITE STATE MACHINE

 

A Finite State Machine has:

- k States S_1, S_2, \dots, S_k (one is the “initial” state)
- m inputs I_1, I_2, \dots, I_m
- n outputs O_1, O_2, \dots, O_n
- Transition Rules, $S'(S_i, I_1, I_2, \dots, I_m)$
for each state and input combination
- Output Rules, $O(S_i)$ for each state

DISCRETE STATE, DISCRETE TIME

 


While a ROM is shown here in the feedback path any form of combinational logic can be used to construct a state machine.


Two design choices:

 - (1) outputs *only* depend on state (Moore)
- (2) outputs depend on inputs + state (Mealy)

s state bits $\rightarrow 2^s$ possible states




STATE TRANSITION DIAGRAMS

 


A state transition diagram is an abstract 'graph' representation of a 'state transition table', where each state is represented as a node and each transition is represented as an arc. It represents the machine's behavior not its implementation!

★ = no buttons pressed

 




EXAMPLE STATE DIAGRAMS

 

MOORE Machine:
Outputs on States

 

MEALY Machine:
Outputs on Transitions

Arcs leaving a state must be:

(1) **mutually exclusive**

can only have one choice for any given input value

(2) **collectively exhaustive**

every state must specify what happens for each possible input combination. "Nothing happens" means arc back to itself.

NEXT TIME



Counting state machines

