



# ALL THE GATES

There are only 16 possible 2-input gates... Let's examine all of them. Some we already know, others are just silly.

I N P U T	Z	A	A	B	X	N	X	N	A	N	B	A	O		
AB	O	D	B	A	A	B	R	R	R	'B'	B	'A'	A	D	E
00	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1
01	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1
10	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1
11	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1

How many of these gates can be implemented using a single CMOS gate?



N-FETs can only pull the output to "0", and only if one or more of their inputs is a "1".

P-FETs can only pull the output to "1", and only if one or more of their inputs is a "0".

Do we really need all of these gates?


Nope! Once we realize that we can describe all of them using just NOT, followed by AND, followed by OR.

# COMPOSING GATES TO BUILD OTHERS




Let's start with a couple of basics, AND and OR. Each can be constructed using a pair of CMOS gates, AND is just NAND with an inverter, and OR is just NOR with an inverted output.

AND	
AB	Y
00	0
01	0
10	0
11	1

 

OR	
AB	Y
00	0
01	1
10	1
11	1

 




These two gates are particularly important. Using them will allow us to develop a systematic approach for constructing any combinational function.



# COMPOSING ARBITRARY GATES

B > A		
AB	Y	
00	0	
01	1	
10	0	
11	0	

XOR		
AB	Y	
00	0	
01	1	
10	1	
11	0	

   

How many different gates do we really need?

We can always do it with 3 different types of gates (AND, OR, INVERT), and sometimes with 2, but, can we use fewer?

The TRICK is to OR the ANDs of all input combinations that generate an output of "1". You don't need the OR gate if only one input combination results in a "1".



You need Inverters to handle input combinations involving "0"s, ANDs, and ORs.

# ONE WILL DO!


NANDs and NORs are UNIVERSAL!

A UNIVERSAL gate is one that can be used to implement \*ANY\* COMBINATIONAL FUNCTION. There are many UNIVERSAL gates, but not all gates are UNIVERSAL



Q: What is a COMBINATIONAL FUNCTION?

 A: Any function that can be written as a truth table.






Ah!, but what if we want more than 2-inputs?

# A FEW MORE GATES



a) OR GATE

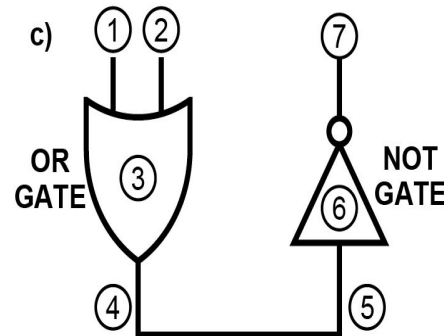  


- Composing gates for high fan-in
- SOP logic synthesis
- MUX logic



# STUPID GATE TRICKS


Suppose we have some 2-input XOR gates:

 

$$t_{pd} = 1 \text{ nS}$$

A	B	C
0	0	0
0	1	1
1	0	1
1	1	0

And we want an N-input XOR:

 


output = 1  
iff number  
of "1"s input is  
ODD ("PARITY")

$$t_{pd} = N \text{ nS} \text{ -- WORST CASE.}$$

Can we compute an N-input XOR faster?


 
# I THINK THAT I SHALL NEVER SEE A GATE LOVELY AS A ...



EVERY N-Input  
Combinational function be  
implemented using only  
2-input gates? But, it's  
handy to have gates with  
more than 2-inputs when  
needed.

N-input TREE has  $O(\log N)$  levels...

Signal propagation takes  $O(\log N)$  gate delays.

# A SYSTEMATIC DESIGN APPROACH



## Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

- 1) Write the functional spec as a truth table
- 2) Write down a Boolean expression for every "1" in the output

$$Y = (!C \&\& !B \&\& A) \parallel (!C \&\& B \&\& A) \parallel (C \&\& B \&\& !A) \parallel (C \&\& B \&\& A)$$

- 3) Wire up the ideal gates, replace them with equivalent realizable gates, call it a day, and go home!

- it's systematic!
- it works!
- it's easy!
- we get to go home!



This approach will **always** give us logic expressions in a particular form:

**SUM-OF-PRODUCTS**






# STRAIGHTFORWARD SYNTHESIS

We can implement

SUM-OF-PRODUCTS

with just 3 levels of logic.

INVERTERS/AND/OR

 





# OTHER USEFUL GATE COMBINATIONS

NAND-NAND

$$\!(A \& \& B) = \!A \parallel \!B$$

 



"Pushing and Cancelling Bubbles"

 

DeMorgan's Laws

NOR-NOR



$$\!(A \parallel B) = \!A \& \& \!B$$

  

# OTHER USEFUL CMOS GATES





## AOI (AND-OR-INVERT)

  

AOI and OAI structures can be realized as a single CMOS gate. However, their function is equivalent to 3 levels of logic.

## OAI (OR-AND-INVERT)

  


An OAI's DeMorgan equivalent is usually easier to think about.


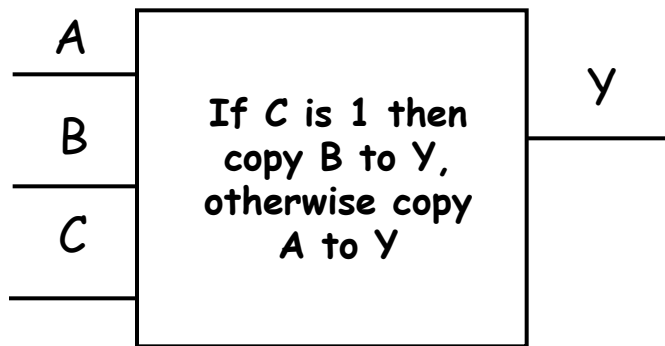
# ANOTHER INTERESTING 3-INPUT GATE





Based on C, select the A or B input to be copied to Y.



## Truth Table

C	B	A	Y
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1



## 2-input Multiplexer

  



# MUX COMPOSITIONS AND SHORTCUTS



A 4-input Mux  
(implemented as a tree)

  

A 4-bit wide 2-input Mux

  



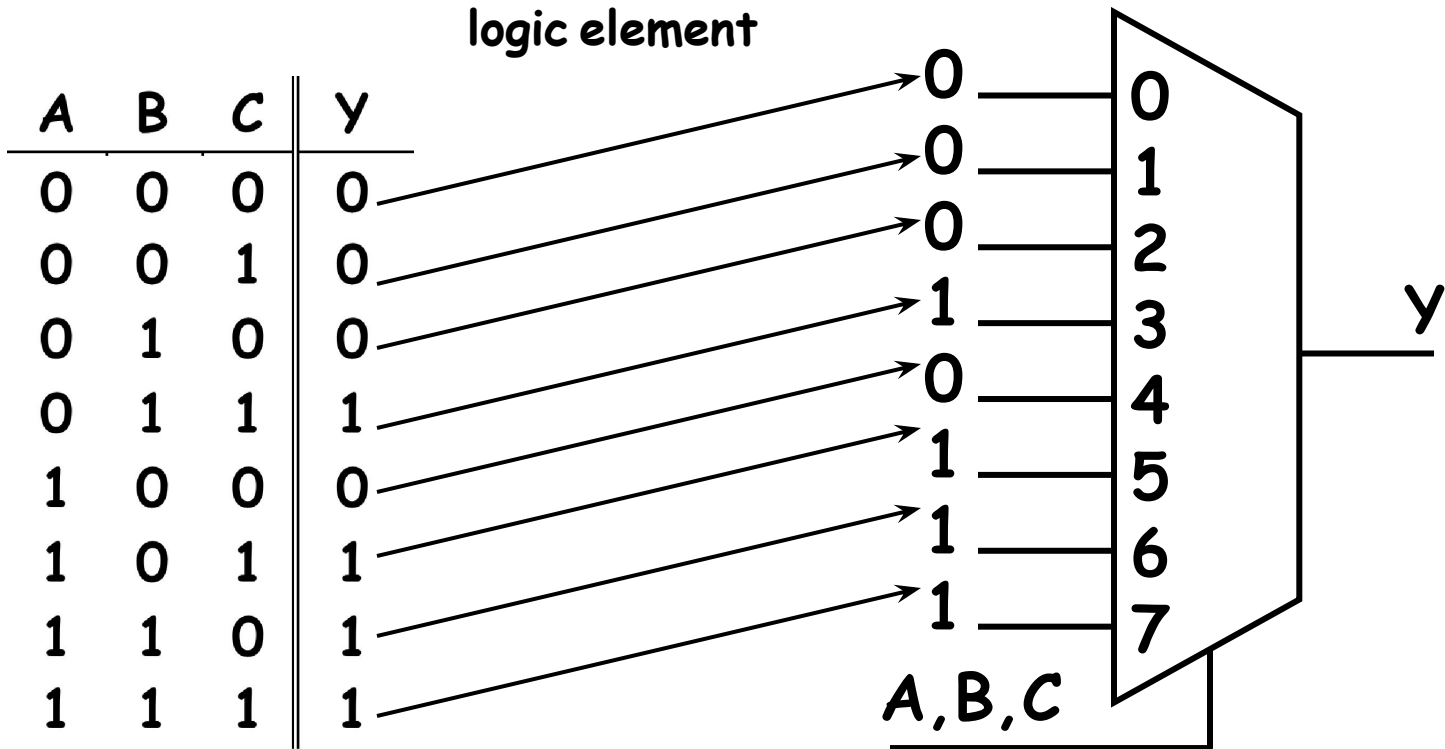
# MUX FUNCTION SYNTHESIS

Consider implementation of some arbitrary Combinational function,  $F(A,B,C)$ ... using a MULTIPLEXER as the only circuit element:

Mux Logic: An example "configurable" logic element






# MUX LOGIC TRICKS

We can apply certain optimizations to MUX Function synthesis

Desired Logic Function

A	B	C	Y
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

- Largely by inspection or exhaustive search



- Build any N-input gate with an N-1 input MUX & one inverter



# NEXT TIME

Binary Circuits that:  
ADD  
SUBTRACT  
SHIFT

