


# BOOLEAN UNIT (THE OBVIOUS WAY)



It is simple to build up a Boolean unit using primitive gates and a mux to select the function.

Since there is no interconnection between bits, this unit can be simply replicated at each position. The cost is about 7 gates per bit. One for each primitive function, and approx 3 for the 4-input mux.

 This is a straightforward, but not elegant design.






# COOLER BOOLS

We can better leverage a MUX's capabilities in our Boolean unit design, by connecting the bits to the select lines.

Why is this better?

While it might take a little logic to decode the truth table inputs, you only have to do it once, independent of the number of bits.

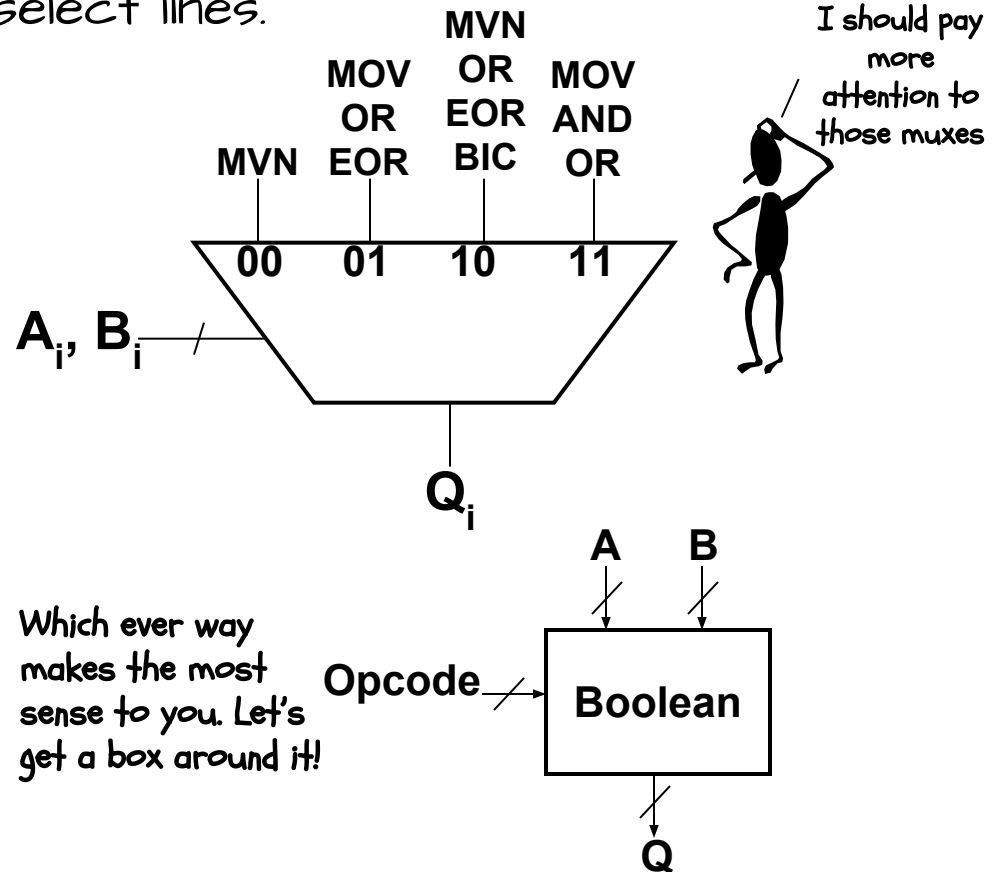BTW, it also handles the MOV and MVN cases.



# DECODING THE BOOLEANS AND OTHERS



It may seem a little tedious, but all the controls that we need can be derived from the ARM OpCode encodings.


The 'X's in the truth table are "don't cares" they provide flexibility in the implementation.

Opcode	Code				00	01	10	11	Sub	Rsb	Math
AND	0	0	0	0	0	0	0	1	X	X	0
EOR	0	0	0	1	0	1	1	0	X	X	0
SUB	0	0	1	0	X	X	X	X	1	0	1
RSB	0	0	1	1	X	X	X	X	0	1	1
ADD	0	1	0	0	X	X	X	X	0	0	1
ADC	0	1	0	1	X	X	X	X	0	0	1
SBC	0	1	1	0	X	X	X	X	1	0	1
RSC	0	1	1	1	X	X	X	X	0	1	1
TST	1	0	0	0	0	0	0	1	X	X	0
TEQ	1	0	0	1	0	1	1	0	X	X	0
<u>CMP</u>	1	0	1	0	X	X	X	X	1	0	1
CMN	1	0	1	1	X	X	X	X	0	0	1
ORR	1	1	0	0	0	1	1	1	X	X	0
MOV	1	1	0	1	0	1	0	1	X	X	0
BIC	1	1	1	0	0	0	1	0	X	X	0
MVN	1	1	1	1	1	0	1	0	X	X	0
 
# AN ALU, AT LAST



We give the "Math Center" of a computer a special name-- the Arithmetic Logic Unit (ALU). For us, it just a big box of gates!






# BINARY MULTIPLICATION

The key to multiplication was memorizing a digit-by-digit table... Everything else was just adding

×	0	1
0	0	0
1	0	1

×	0	1	2	3	4	5	6	7	8	9
0	0	0	0	0	0	0	0	0	0	0
1	0	1	2	3	4	5	6	7	8	9
2	0	2	4	6	8	10	12	14	16	18
3	0	3	6	9	12	15	18	21	24	27
4	0	4	8	12	16	20	24	28	32	36
5	0	5	10	15	20	25	30	35	40	45
6	0	6	12	18	24	30	36	42	48	54
7	0	7	14	21	28	35	42	49	56	63
8	0	8	16	24	32	40	48	56	64	72
9	0	9	18	27	36	45	54	63	72	81

 


You've got to be kidding... It can't be that easy



# WARM UP / REVIEW

Suppose that you wanted to extend the ARM ISA to include a **nor** instruction like MIPS, how would the mux inputs of the BOOL functional block shown on the right be set?

 - A)  $X, Y, Z = 1, W = 0$
- B)  $X = 0, Y, Z, W = 1$
- C)  $X = \text{NOT}(\text{OR}(A_i, B_i)), Y, Z, W = 0$
- D)  $X = 1, Y, Z, W = 0$
- E) A NOR cannot be implemented with this functional block





# DIGIT BY DIGIT = BIT BY BIT

The "Binary" Multiplication Table

X	0	1
0	0	0
1	0	1

Hey, that looks like an AND gate



Binary multiplication is implemented using the same basic longhand algorithm that you learned in grade school.

$$\begin{array}{r}
 A_3 \quad A_2 \quad A_1 \quad A_0 \\
 \times B_3 \quad B_2 \quad B_1 \quad B_0 \\
 \hline
 \end{array}$$

$A_j B_i$  is a "partial product"

$$\begin{array}{r}
 \longrightarrow A_3 B_0 \quad A_2 B_0 \quad A_1 B_0 \quad A_0 B_0 \\
 \quad \quad A_3 B_1 \quad A_2 B_1 \quad A_1 B_1 \quad A_0 B_1 \\
 \quad \quad \quad A_3 B_2 \quad A_2 B_2 \quad A_1 B_2 \quad A_0 B_2 \\
 + \quad \quad \quad \quad A_3 B_3 \quad A_2 B_3 \quad A_1 B_3 \quad A_0 B_3 \\
 \hline
 \end{array}$$

Easy part: forming partial products (just an AND gate since  $B_i$  is either 0 or 1)

Hard part: adding M, N-bit partial products

Multiplying N-digit number by M-digit number gives (N+M)-digit result




# MULTIPLYING IN ASSEMBLY

One can use this "Shift and Add" approach to write a multiply function in assembly language:

```

; multiplies r0 and r1
mult:  mov    r3,#0          ; zero product
part:  tst    r1,#1          ; check if least significant bit=1
       addne r3,r3,r0      ; add multiplicand to product
       mov   r0,r0,lsr #1  ; multiplicand *= 2
       movs  r1,r1,lsr #1  ; multiplier /= 2
       bne   part         ; continue while multiplier is not 0
       mov   r0,r3         ; copy product to return value
       bx   lr

```

 

Hum, maybe we could do something more clever.







# MULTIPLIER UNIT-BLOCK



We introduce a new abstraction to aid in the construction of multipliers called the "Unsigned Multiplier Unit-block"

We did a similar thing last lecture when we converted our adder to an add/subtract unit.

$A_k$  are bits of the Multiplicand and  $B_i$  are bits of the Multiplier.

The  $P_{i,k}$  inputs and outputs represent "partial products" which are partial results from adding together shifted instances of the Multiplicand.

The initial  $P_{0,k}$  is zero.

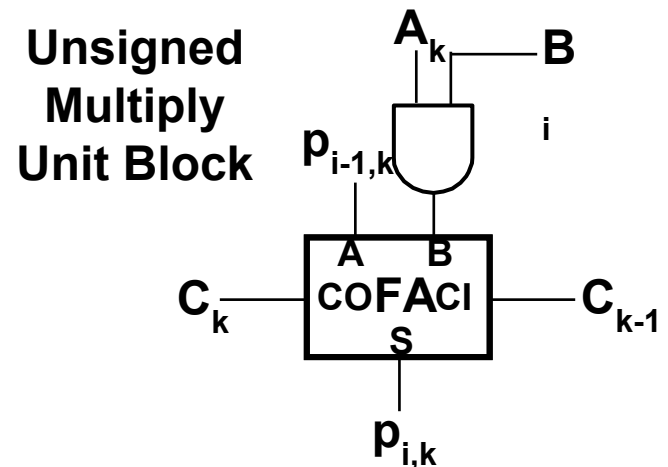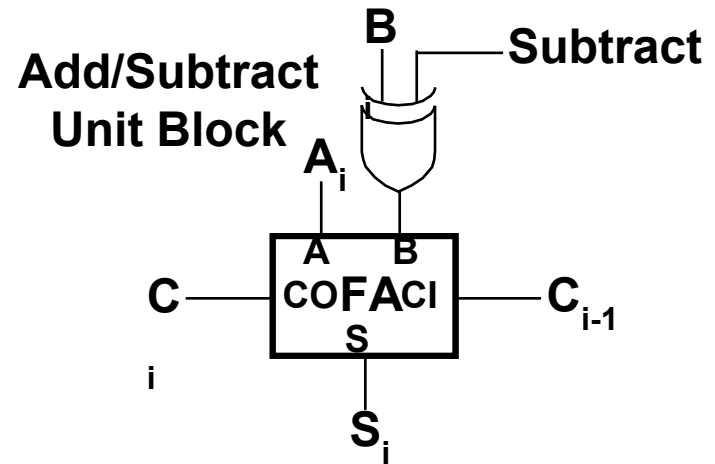

# SIMPLE COMBINATIONAL MULTIPLIER



$$t_{PD} = 10 * t_{PD}$$


not 16

$$t_{PD} = (2*(N-1) + N) * t_{PD}$$

Components

$N * HA$

$N(N-1) * FA$

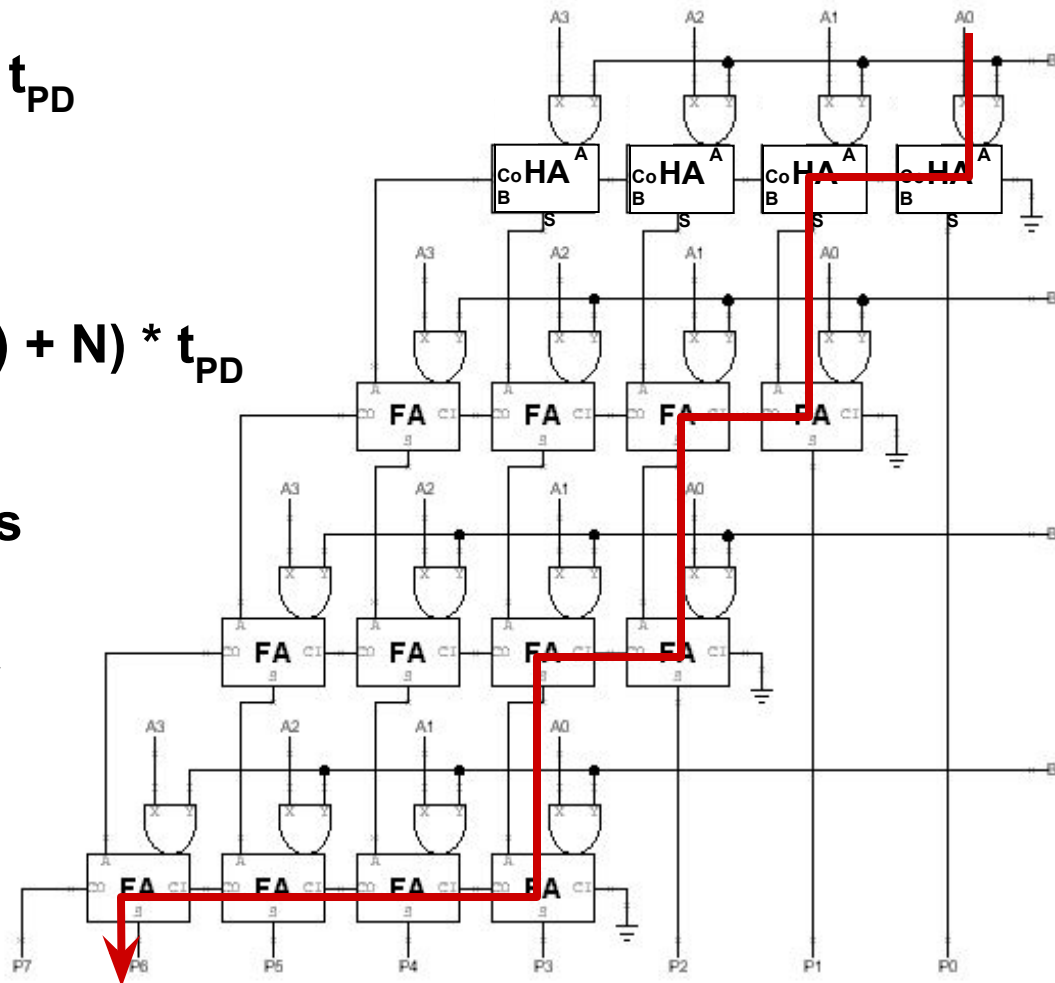

Is this faster than our assembly code?

To determine the timing specification of a composite combinational circuit we find the worst-case path for every output to any input.



NB: this circuit only works for nonnegative operands



# "CARRY-SAVE" MULTIPLIER

Observation: Rather than propagating the carries to the next adder in each row, they can instead be forwarded to the next column of the following row


$$t_{PD} = 8 * t_{PD}$$

$$t_{PD} = (N+N) * t_{PD}$$

Components

~~$N * HA$~~

$N^2 * FA$

 

These Adders can be removed, and the AND gate outputs tied directly to the Carry inputs of the next stage.


This small performance improvement hardly seems worth the effort, however, this design is easier to "pipeline".




 
# HIGHER-RADIX MULTIPLICATION

Idea: If we could use, say, 2 bits of the multiplier in generating each partial product we would **halve the number of rows and halve the latency of the multiplier!**



**Booth's insight: rewrite  $2*A$  and  $3*A$  cases, leave  $4A$  for next partial product to do!**

$$\begin{aligned}
 B_{K+1,K} * A &= 0 * A \Rightarrow 0 \\
 &= 1 * A \Rightarrow A \\
 &= 2 * A \Rightarrow 2A \text{ or } 4A - 2A \\
 &= 3 * A \Rightarrow 4A - A
 \end{aligned}$$



# BOOTH RECODING OF MULTIPLIER

current bit pair from previous bit pair

	$B_{2K+1}$	$B_{2K}$	$B_{2K-1}$	action	
-89 = <span style="border: 1px solid red; padding: 2px;">1 0 1 0 0 1 1 1 . 0</span>	0	0	0	add 0	
= -1 * 2 <sup>0</sup> (-1)	0	0	1	add A	
+ 2 * 2 <sup>2</sup> (8)	0	1	0	add A	
+ (-2) * 2 <sup>4</sup> (-32)	0	1	1	add 2*A	
+ (-1) * 2 <sup>6</sup> (-64)	1	0	0	sub 2*A	
-89	1	0	1	sub A	
	1	1	0	sub A	← -2*A+A
	1	1	1	add 0	← -A+A

An encoding where each bit has the following weights:

$$W(B_{2K+1}) = -2 * 2^{2K}$$

$$W(B_{2K}) = 1 * 2^{2K}$$

$$W(B_{2K-1}) = 1 * 2^{2K}$$

Hey, isn't that a negative number?



Yep! Booth recoding works for 2-Complement integers, now we can build a signed multiplier.

A "1" in this bit means the previous stage needed to add 4\*A. Since this stage is shifted by 2 bits with respect to the previous stage, adding 4\*A in the previous stage is like adding A in this stage!



# BOOTH MULTIPLIER UNIT BLOCK


Logic surrounding each basic adder:

- Control lines (x2, Sub, Zero)  
Are shared across each row
- Must handle the "+1" when Sub is 1  
(extra half adders in a carry-save array)

## NOTE:

- Booth recoding can be used to implement signed multiplications



$B_{2K+1}$	$B_{2K}$	$B_{2K-1}$	x2	Sub	Zero
0	0	0	X	X	1
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	1	0	0
1	0	0	1	1	0
1	0	1	0	1	0
1	1	0	0	1	0
1	1	1	X	X	1

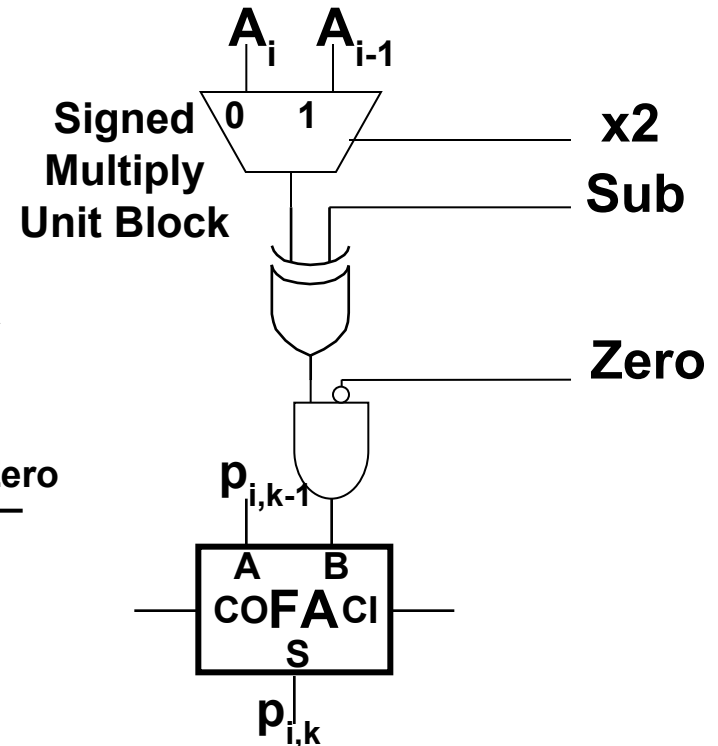


 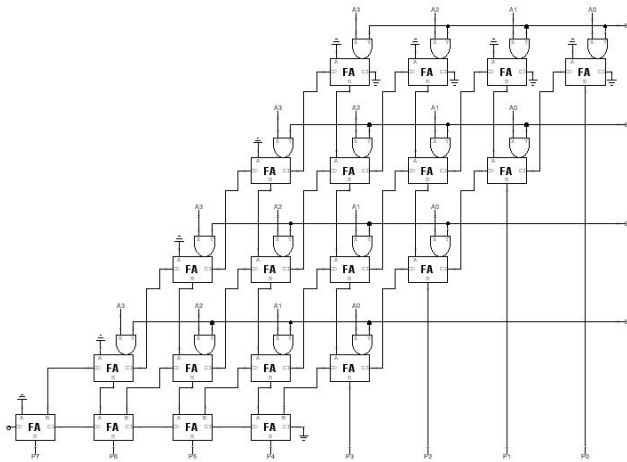
# BIGGER MULTIPLIERS

- Using the approaches described we can construct multipliers of arbitrary sizes, by considering every adder at the "bit" level
- We can also, build bigger multipliers using smaller ones




- Considering this problem at a higher-level leads to more "non-obvious" optimizations


 
# CAN WE MULTIPLY WITH LESS?

- How many operations are needed to multiply 2, 2-digit numbers?
- 4 multipliers  
4 Adders
- This technique generalizes
  - You can build an 8-bit multiplier using 4 4-bit multipliers and 4 8-bit adders
  - $O(N^2 + N) = O(N^2)$








# $O(N^2)$ MULTIPLIER LOGIC

The functional blocks look like

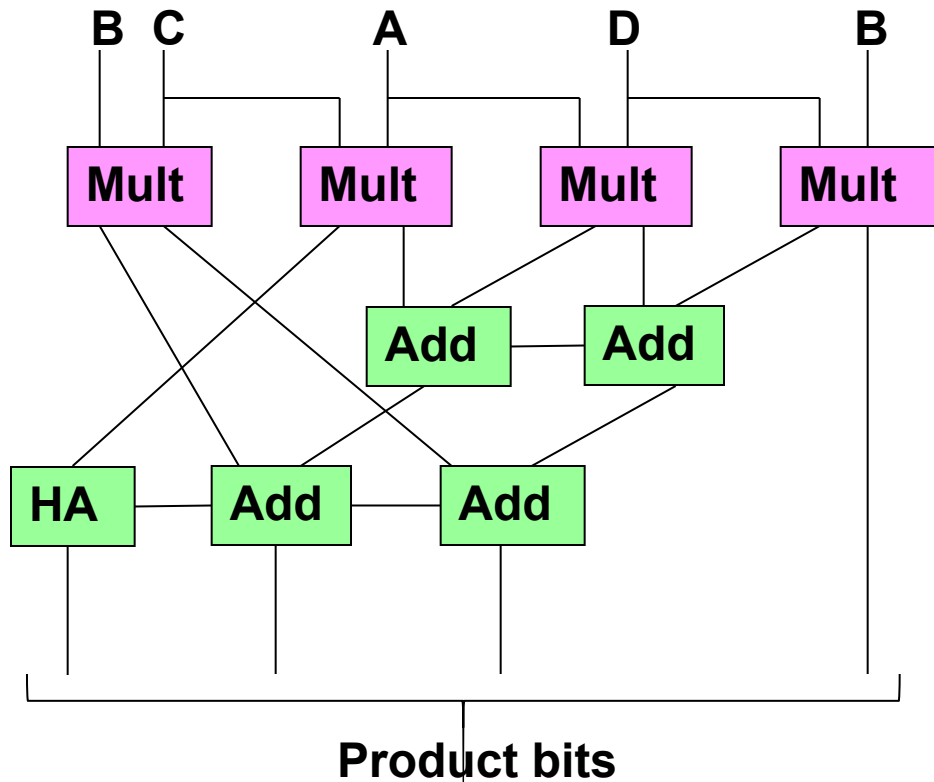

```
  AB
x  CD
-----
  DB
 DA
 CB
 CA
```



# A TRICK

- The two middle partial products can be computed using a single multiplier and other partial products
- $DA + CB = (C + D)(A + B) - (CA + DB)$
- 3 multipliers  
8 adders
- This can be applied recursively  
(i.e. applied within each partial product)
- Leads to  $O(N^{1.58})$  adders
- This trick is becoming more popular as  $N$  grows. However, it is less regular, and the overhead of the extra adders is high for small  $N$

$$\begin{array}{r}
 \phantom{x} \quad \quad \quad \text{AB} \\
 \text{x} \quad \quad \quad \text{CD} \\
 \hline
 \phantom{x} \quad \quad \quad \text{DB} \\
 \phantom{x} \quad \quad \quad \text{DA} \\
 \phantom{x} \quad \quad \quad \text{CB} \\
 \phantom{x} \quad \quad \quad \text{CA}
 \end{array}$$



# LET'S TRY IT BY HAND

1) Choose 2, 2 digit numbers to multiply:  $ab \times cd$

$$42 \times 37$$

2) Multiply digits:  $p1 = a \times c$ ,  $p2 = b \times d$ ,  $p3 = (c + d)(a + b)$


$$p1 = 4 \times 3 = 12, p2 = 2 \times 7 = 14, p3 = (4+2) \times (3+7) = 60$$

3) Compute partial subtracted sum,  $SS = p3 - (p1 + p2)$

$$SS = 60 - (12 + 14) = 34$$

 4) Add as follows:  $p = 100 \times p1 + 10 \times SS + p2$

$$P = 1200 + 340 + 14 = 1554 = 42 \times 37$$






# AN $O(N^{1.58})$ MULTIPLIER

The functional blocks would look like:

$$\begin{array}{r}
 \quad \quad AB \\
 \times \quad CD \\
 \hline
 \quad \quad DB \\
 \quad \quad SS \\
 \quad \quad CA
 \end{array}$$

Where
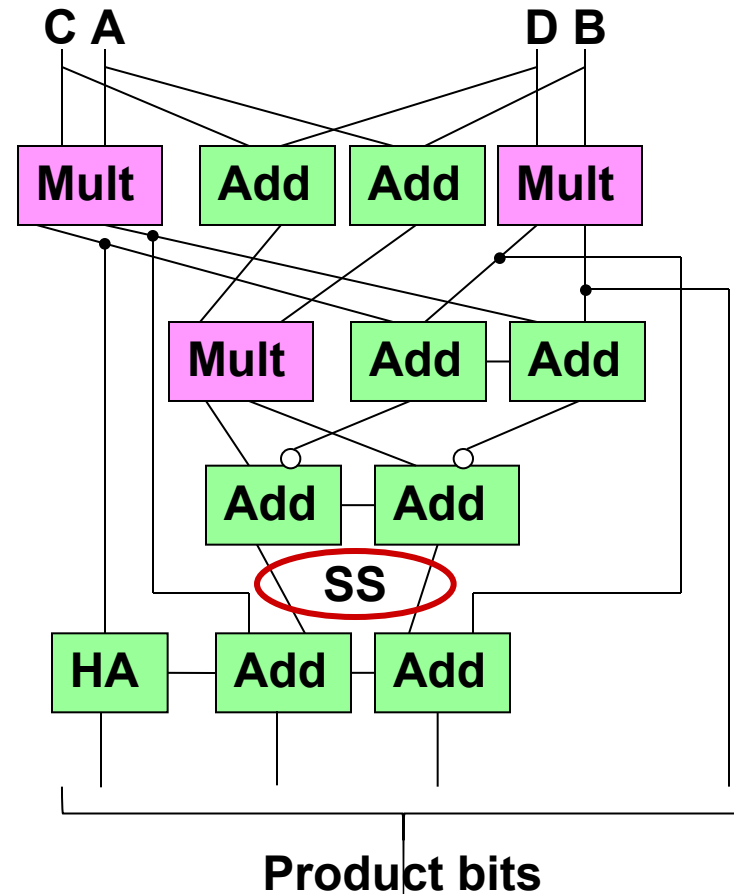
$$\begin{aligned}
 SS &= (C+D)(A+B) \\
 &\quad - (CA+DB)
 \end{aligned}$$



Note: Adders with a bubble on one of their inputs becomes a subtractor in this notation.

