 


SYNCHRONOUS LOGIC




- 1) Sequential Logic
- 2) Synchronous Design
- 3) Synchronous Timing Analysis
- 4) Single Clock Design
- 5) Finite State Machines
- 6) Mealy and Moore
- 7) State Transition Diagrams





ROAD TRAVELED SO FAR..

 

Combinational contract:

- Voltage-based "bits"
- 1-bit per wire
- Generate quality outputs, tolerate inferior inputs
- Combinational contract
- Complete in/out/timing spec

Acyclic connections

Composable blocks

Design:

- truth tables
- sum-of-products
- muxes
- ROMs

Storage & state

Dynamic discipline

Finite-state machines

Throughput & latency


Pipelining

Our motto: Sweat the details once, and then put a box around it!



SOMETHING WE CAN'T BUILD

 What if you were given the following system design specification?




What makes this System so different from those we've discussed before?

1. "State" - i.e. the circuit has memory
2. The output was changed by a input "event" (pushing a button) rather than an input "value"




"SEQUENTIAL" = STATEFUL

 


Plan: Build a Sequential Circuit with stored digital STATE -

- MEMORY stores CURRENT state
- Combinational Logic computes
 - the NEXT state (Based on inputs & current state)
 - the OUTPUTs (Based on inputs and/or current state)
 - State changes on LOAD control input

 Didn't we develop some memory devices last time?



"SYNCHRONOUS" SINGLE-CLOCK LOGIC

 


Questions for register-based designs:

- How much time for useful work (i.e. for combinational logic delay)?

- Does it help to guarantee a minimum t_{CD} ? How 'bout designing registers so that

$$t_{CD,reg} \geq t_{HOLD,reg}?$$

 - What happens if CLK signal doesn't arrive at the two registers at exactly the same time (a phenomenon known as "clock skew")?




$$t_1 = t_{CD,reg1} + t_{CD,L} \geq t_{HOLD,reg2}$$

$$t_2 = t_{PD,reg1} + t_{PD,L} \leq t_{CLK} - t_{SETUP,reg2}$$

$$\text{Minimum Clock Period : } t_{CLK} \geq t_{PD,reg1} + t_{PD,L} + t_{SETUP,reg2}$$



EXAMPLE: SYNCHRONOUS TIMING

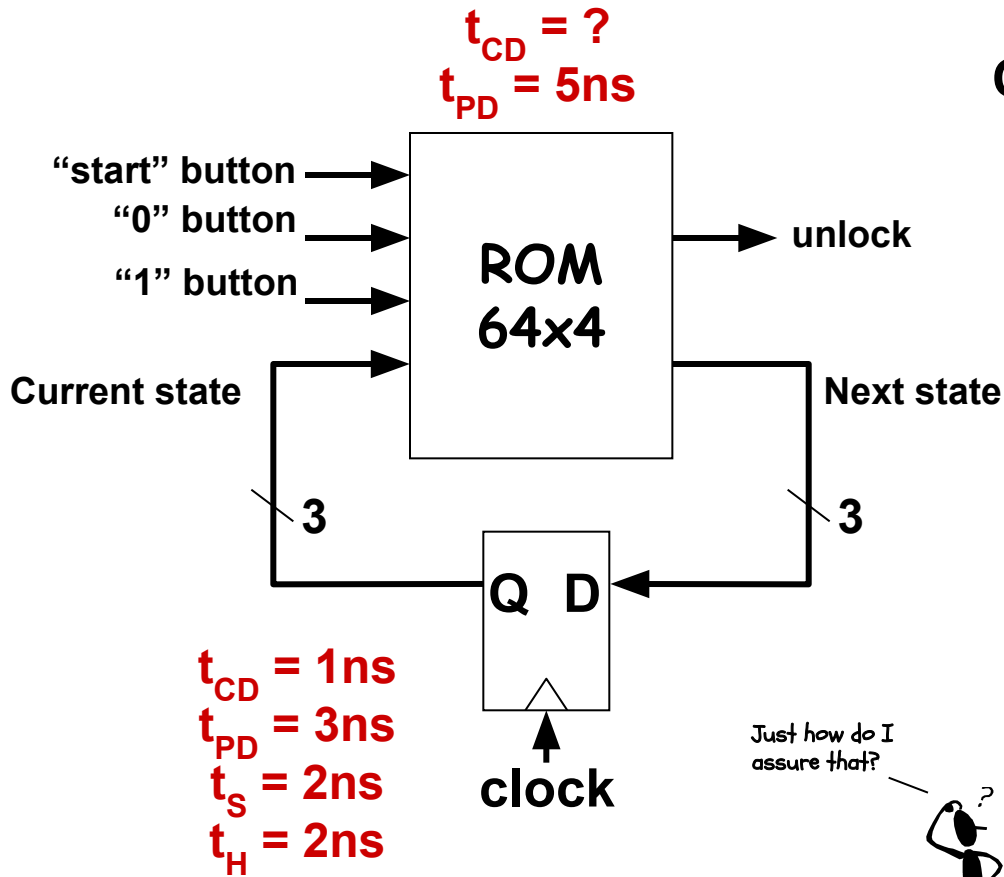

Questions:

1. t_{CD} for the ROM?

$$t_{CD,REG} + t_{CD,ROM} > t_{H,REG}$$

$$1 ns + t_{CD,ROM} > 2 ns$$

$$t_{CD,ROM} > 1 ns$$

2. Min. clock period?

$$t_{CLK} > t_{PD,REG} + t_{PD,ROM} + t_{S,REG}$$

$$t_{CLK} > 3 ns + 5 ns + 2 ns$$

$$t_{CLK} > 10 ns$$

3. Constraints on inputs?

“start”, “0”, and “1” must be valid

$t_{PD,ROM} + t_{S,REG} = 5 + 2 = 7 ns$
before the clock and held

$t_{H,REG} - t_{CD,ROM} = 2 - 1 = 1 ns$
after it.

Just how do I
assure that?




SYNCHRONOUS SINGLE-CLOCK DESIGN



Sequential \neq Synchronous

 However, Synchronous = A recipe for robust sequential circuits:



- No combinational cycles
(other than those already inside the registers)
- Only cares about values of combinational circuits just before rising edge of clock
- Clock period greater than every combinational delay
- Changes state after all logic transitions have stopped!




DESIGNING SEQUENTIAL LOGIC


Sequential logic is used when the solution to some design problem involves a *sequence of steps*:

How to open digital combination lock w/ 3 buttons ("start", "0" and "1"):

 - Step 1: press "start" button
- Step 2: press "0" button
- Step 3: press "1" button
- Step 4: press "1" button
- Step 5: press "0" button



 Information remembered between steps is called **state**. Might be just what step we're on, or might include results from earlier steps we'll need to complete a later step.





IMPLEMENTING A "STATE MACHINE"

This flavor of "truth-table" is called a "state-transition table"


This is starting to look like a PROGRAM




Current State	"start"	"1"	"0"	Next State	unlock
---	1	---	---	start	0 000
start	000	0	0	1	digit1 0 001
start	000	0	1	0	error 0 101
start	000	0	0	0	start 0 000
digit1	001	0	1	0	digit2 0 010
digit1	001	0	0	1	error 0 101
digit1	001	0	0	0	digit1 0 001
digit2	010	0	1	0	digit3 0 011
...					
digit3	011	0	0	1	unlock 0 100
...					
unlock	100	0	1	0	error 1 101
unlock	100	0	0	1	error 1 101
unlock	100	0	0	0	unlock 1 100
error	101	0	---	---	error 0 101

6 different states → encode using 3 bits

NOW, WE DO IT WITH HARDWARE!

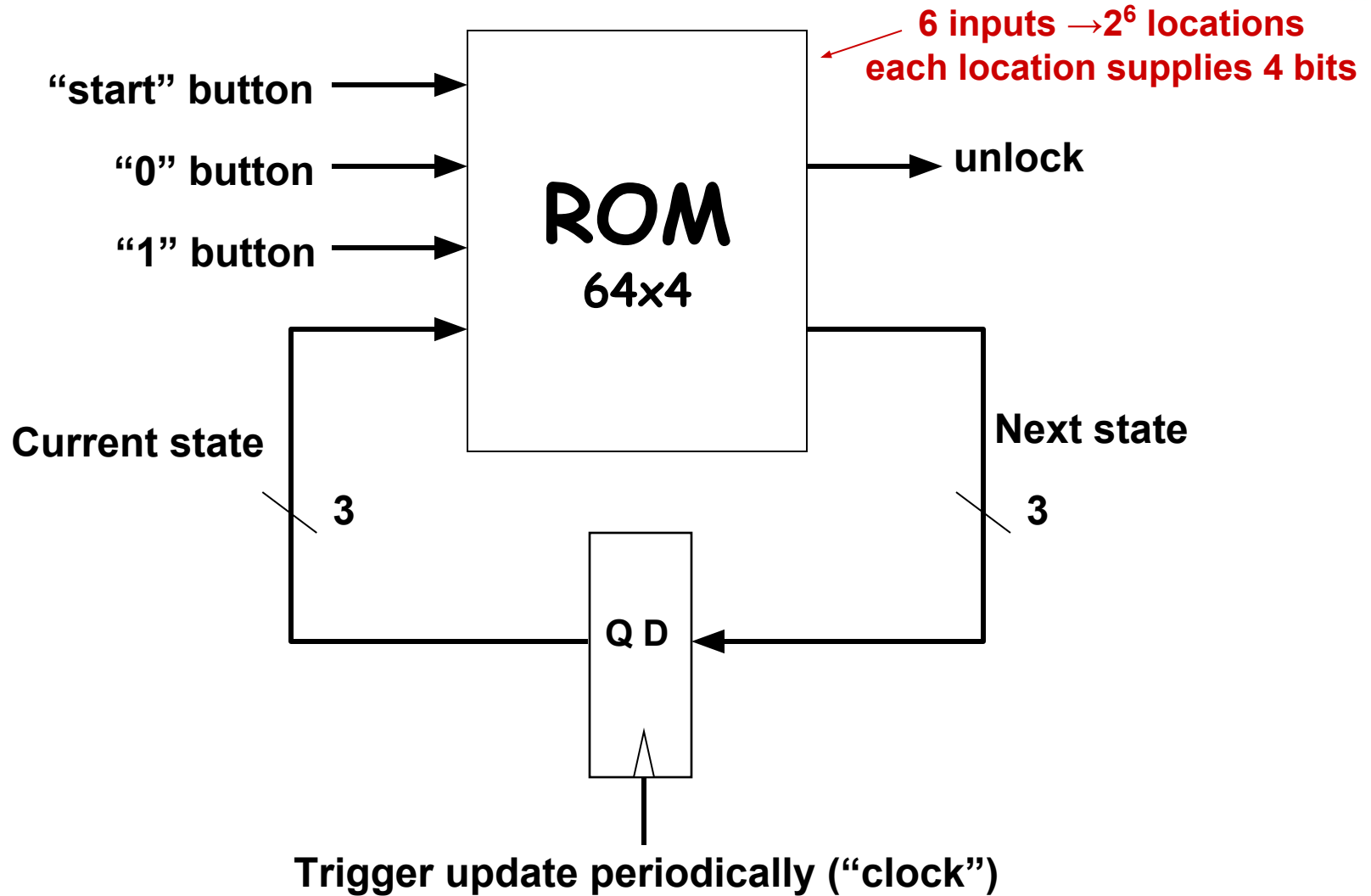

A FINITE STATE MACHINE

 


A Finite State Machine has:

- k States S_1, S_2, \dots, S_k (one is the “initial” state)
- m inputs I_1, I_2, \dots, I_m
- n outputs O_1, O_2, \dots, O_n
- Transition Rules, $S'(S_i, I_1, I_2, \dots, I_m)$
for each state and input combination
- Output Rules, $O(S_i)$ for each state



DISCRETE STATE, DISCRETE TIME

 


While a ROM is shown here in the feedback path any form of combinational logic can be used to construct a state machine.

Two design choices:

 
- (1) outputs *only* depend on state (Moore)
- (2) outputs depend on inputs + state (Mealy)

s state bits $\rightarrow 2^s$ possible states






STATE TRANSITION DIAGRAMS

 


A state transition diagram is an abstract 'graph' representation of a 'state transition table', where each state is represented as a node and each transition is represented as an arc. **It represents the machine's behavior not its implementation!**

★ = no buttons pressed

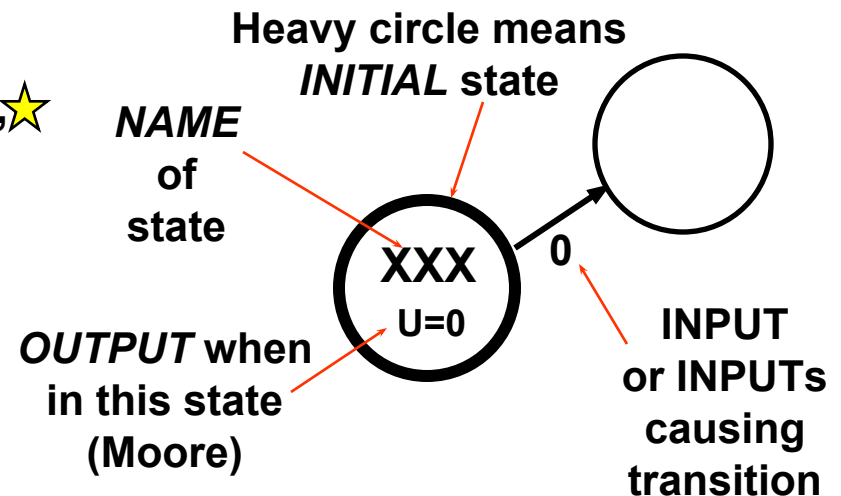




EXAMPLE STATE DIAGRAMS

 

MOORE Machine:
Outputs on States

 

MEALY Machine:
Outputs on Transitions

Arcs leaving a state must be:

(1) **mutually exclusive**

can only have one choice for any given input value

(2) **collectively exhaustive**

every state must specify what happens for each possible input combination. "Nothing happens" means arc back to itself.

NEXT TIME



Counting state machines

